


# CSC 411

Computer Organization (Spring 2024)  
Lecture 19: Introduction to logic design

Prof. Marco Alvarez, University of Rhode Island
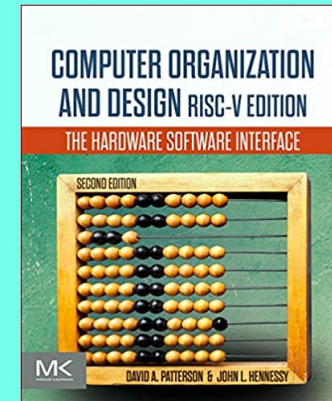
## Disclaimer


Some figures and slides are adapted from:  
Computer Organization and Design (Patterson and Hennessy)  
The Hardware/Software Interface



## Practice

- Which gate is this?
- not, or, and, xnor, xor, nand, nor


A	B	Y
0	0	
0	1	
1	0	
1	1	

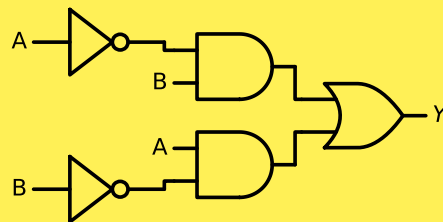
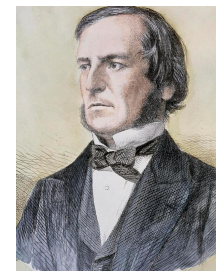
## Boolean algebra

- Uses 1s and 0s
- Defines properties, laws and theorems
  - useful for manipulating and simplifying boolean expressions
  - critical for digital design

George Boole (1815–1864) was an English mathematician, philosopher, and logician. He is best known as the author of *The Laws of Thought* (1854) which contains Boolean algebra, laying the foundations for the Information Age.



[https://en.wikipedia.org/wiki/George\\_Boole](https://en.wikipedia.org/wiki/George_Boole)

The following slides are just a brief introduction to boolean algebra, not covering all topics in the field, there are many more complex concepts and applications that are beyond the scope of this brief overview.

## Axioms

*identity*

$$1x = x$$

$$x + 0 = x$$

*complementary*

$$xx' = 0$$

$$x + x' = 1$$

*commutative*

$$xy = yx$$

$$x + y = y + x$$

*distributive*

$$x(y + z) = xy + xz$$

$$x + yz = (x + y)(x + z)$$

*associative*

$$(xy)z = x(yz)$$

$$(x + y) + z = x + (y + z)$$

<https://introcs.cs.princeton.edu/java/71boolean/>

## Deriving laws

*negation*

$$0' = 1$$

$$1' = 0$$

*double negation*

$$(x')' = x$$

*annihilation*

$$0x = 0$$

$$1 + x = 1$$

*absorption*

$$x(x + y) = x$$

$$x + xy = x$$

*DeMorgan's laws*

$$(xy)' = x' + y'$$

$$(x + y)' = x'y'$$

<https://introcs.cs.princeton.edu/java/71boolean/>

## Sum of products


▸ Starting from a truth table ...

- any boolean function can be represented with an expression that uses AND, OR, and NOT operators

▸ a.k.a. DNF (disjunctive normal form)

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

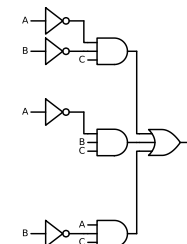
$$Y = \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}C$$



always  
two-level  
logic
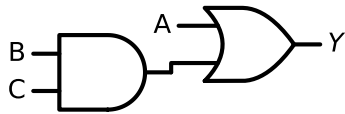
## Simplifying sums of products

$$\begin{aligned}
 Y &= \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C + AB\overline{C} + ABC \quad \text{canonical form} \\
 &= \overline{A}BC + A\overline{B}(\overline{C} + C) + AB(\overline{C} + C) \\
 &= \overline{A}BC + A\overline{B} + AB \\
 &= \overline{A}BC + A(\overline{B} + B) \\
 &= \overline{A}BC + A \\
 &= BC + A \quad \text{minimal form}
 \end{aligned}$$



A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Boolean algebra also defines product of sums, i.e., expressing a function as the product of sums of literals. Both sums of products and products of sums are canonical forms used to simplify and represent Boolean expressions.

## Practice

- Simplify this function


$$Y = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$$

## Building logic circuits
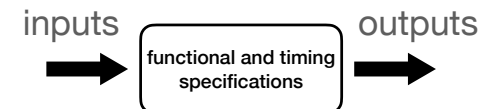
## Logic circuits

- Composition

- inputs and outputs
- functional specification
  - mapping between inputs and outputs (same inputs produce same outputs every time)
  - represented by (usually simplified) boolean expressions, different expressions lead to different design (hardware area, cost, latency, power, etc.)
- timing specification
  - latency between inputs changing and outputs responding



- Types


- **Combinational logic**
  - elements operate on data, output is a function of the inputs, memoryless
- **State (sequential) logic**
  - elements store information, outputs determined by memory and current inputs

# Decoders

## Decoder
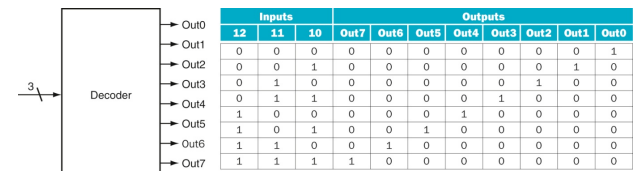
### ▸ Input pattern detector

- combinational logic circuits that convert binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines
- only one of the output lines is active (equal to 1) at any given time, while all the others are 0
- decoders are used for tasks like memory addressing, or interpreting opcodes



a. A 3-bit decoder


Inputs			Outputs							
I2	I1	I0	Out7	Out6	Out5	Out4	Out3	Out2	Out1	Out0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

b. The truth table for a 3-bit decoder

## Practice

### ▸ Complete the following truth table

A	B	Y1	Y2	Y3	Y4
0	0				
0	1				
1	0				
1	1				

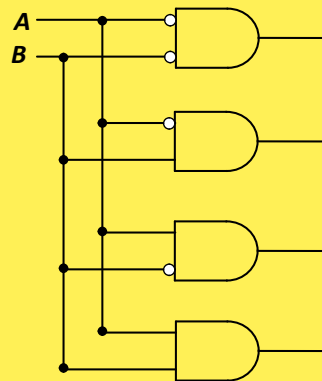


## Multiplexers

# Multiplexer (MUX)

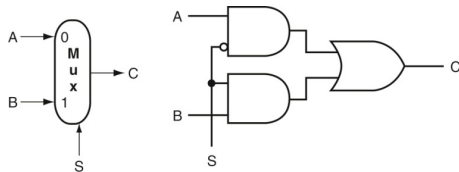
## Selector

- combinational logic circuit , a device that selects one of several input signals and forwards it to a single output line
- selection of the input is controlled by a set of selection lines, which determine which input gets transmitted to the output
- commonly used in data selection, address decoding, etc.



2-to-1 mux

## 4-to-1 mux


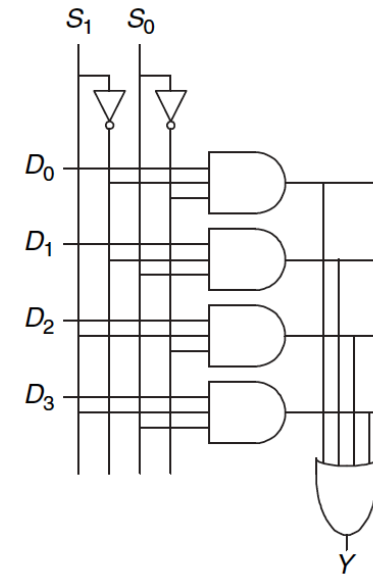


Credit: Digital Design & Computer Architecture, Our Mutlu, ETH, 2023


## Practice

### Complete the following truth table

S	A	B	Y

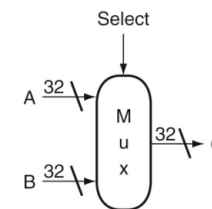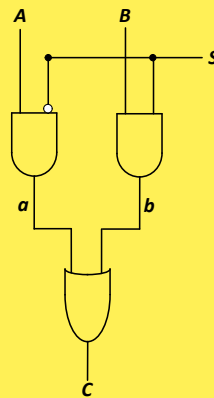

a. A 32-bit wide 2-to-1 multiplexer

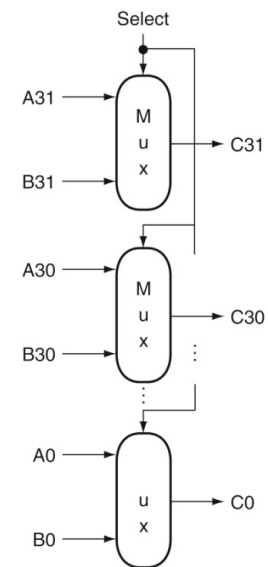

b. The 32-bit wide multiplexer is actually an array of 32 1-bit multiplexers