

# CSC 411

Computer Organization (Spring 2024)  
Lecture 21: ALUs

Prof. Marco Alvarez, University of Rhode Island

# Adder


## 1-bit half-adder

- For now, let's ignore the carry-in (half-adder)
- just add two bits and calculate the output/carry-out

Write a boolean expression for  $C_{out}$ ?


A	B	$C_{out}$	S
0	0		
0	1		
1	0		
1	1		

Write a boolean expression for Sum?

 

## 1-bit adder


- Now considering carry-in

 


Write a boolean expression for  $C_{out}$ ?

Write a boolean expression for Sum?

A	B	$C_{in}$	$C_{out}$	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 


## 4-bit adder

 

 
## Delays in combinational circuits

- Circuit continually responds to input changes
- Outputs are calculated after some **delay**


 
## Example: bit equality

- What is the delay?
- assume NOT takes 1.1 units of time, AND takes 3.9, and OR takes 4.5



The delay of a circuit is determined by its “critical path”, the path between an input and output with the maximum delay

Image credit: CSC 252: Computer Organization: Lecture 11, University of Rochester

## Example: 64-bit equality

- What is the total delay?


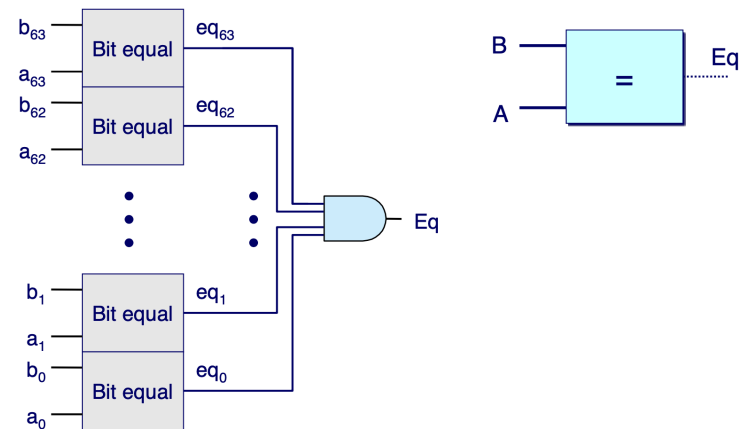



Image credit: CSC 252: Computer Organization: Lecture 11, University of Rochester

# ALUs


## 1-bit ALU that performs AND and OR

 


## 1-bit ALU (AND, OR, Add)

 

## 32-bit ALU

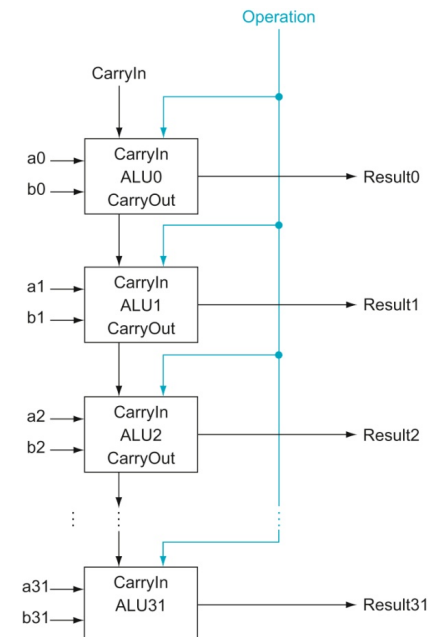

## 1-bit ALU (AND, OR, Add, Sub)

 

Subtraction: Invert and set CarryIn = 1

## 1-bit ALU (AND, OR, Add, Sub, NOR)


We can also add a NOR function.

Instead of adding a separate gate for NOR, we can reuse the hardware.

The insight comes from:

$$\overline{a + b} = \overline{a} \cdot \overline{b}$$


What would be the control bits for NOR?

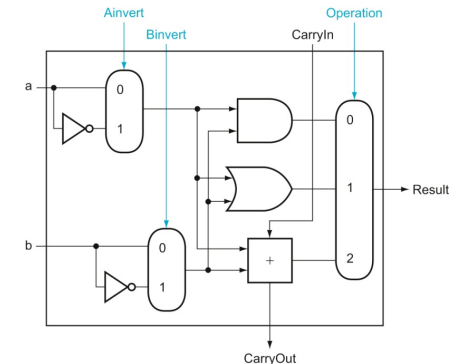

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract

## Overflow detection

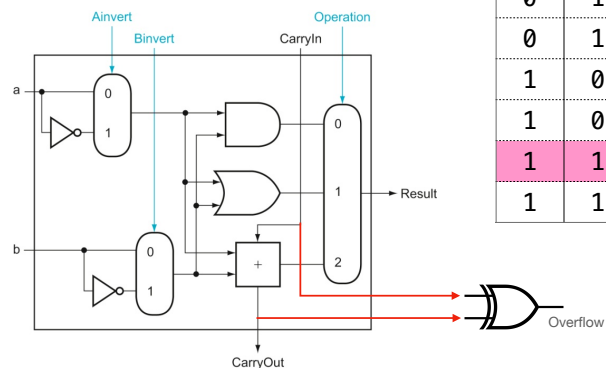**C<sub>in</sub> of MSB != C<sub>out</sub> of MSB**



A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


## Adding SLT

**Set less than** instruction (1 if rs1 < rs2, and 0 otherwise)

Output should be all zeros, with the least significant bit set according to the comparison.

If the ALU performs a-b and we select 3 in the multiplexor, then Result = 0...001 if a < b, and Result = 0...000 otherwise.


MSB

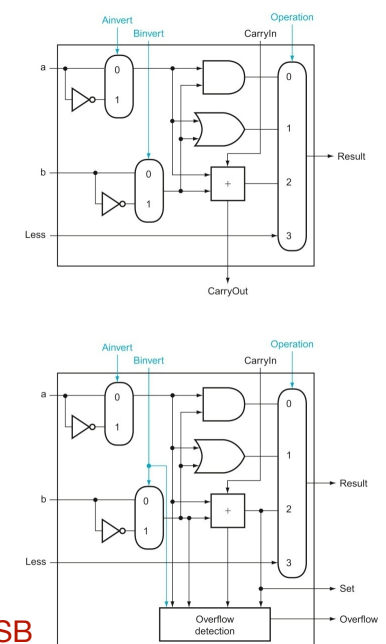
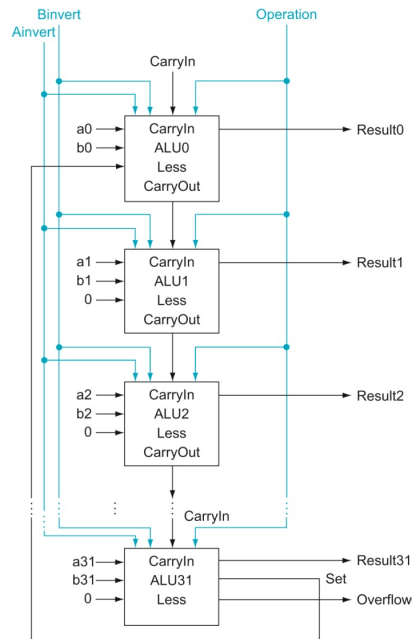
## 32-bit ALU


This is a 32 bit “ripple carry” ALU, connecting 32 1-bit ALUs sequentially.

The **Less** inputs are 0 except for the LSB, which is connected to the **Set** output of the MSB.


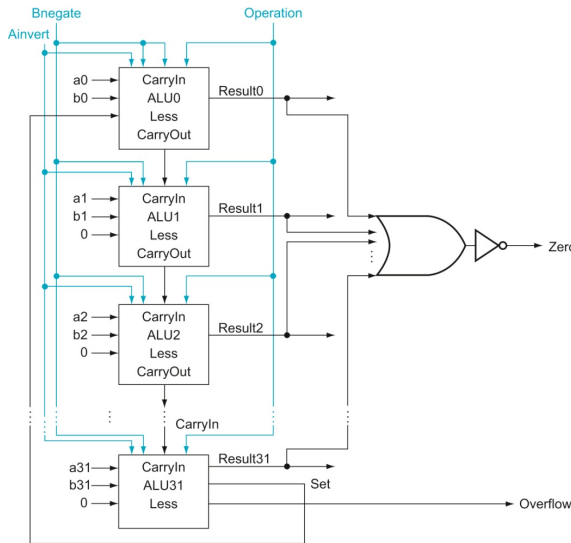
## Adding a zero detector


Checking if two inputs contain the same values (as in **beq**) can be done by performing **a-b** and checking the result is **all zeros**.




## 32-bit ALU

A	Ainv	Bin	Op
and			
or			
add			
sub			
nor			
nand			
slt			
beq			

Control lines?

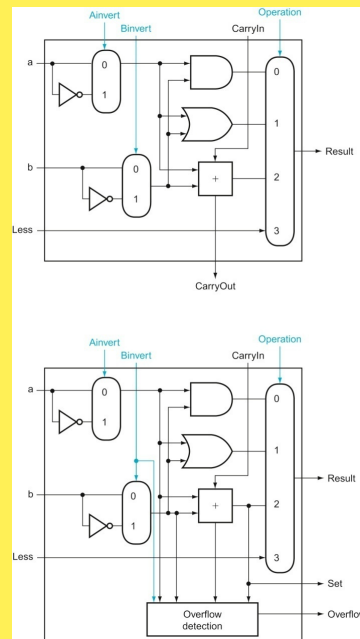

## 32-bit ALU

 

## Ripple carry

### ▸ Total delay?

- the time to go through  $32 \cdot d$  gates!

### ▸ Any logic equation can be expressed as the sum of products

- technically, it should be possible to compute the result by going through only 2 gates
- **caveat:** need many parallel gates and each gate may have a very large number of inputs

### ▸ Can we find a compromise?

- moderate number of gates and inputs to each gate
- moderate number of sequential gates traversed

## 32-bit carry look-ahead adder

Eight 4-bit ALUs using carry lookahead to form a 32-bit adder

Takes less sequential steps than a ripple carry adder

